

Experiment 4

S A Aravind Eswar and Eshan Sharma

1 AIM

To study and analyze the transient response of an LC circuit, determine the natural frequency (Ω_n), and calculate the damping ratio (ξ) using theoretical and experimental methods.

2 MATERIALS AND APPARATUS REQUIRED

- 1) 100 μ F Capacitor
- 2) Largest available inductor in the lab (denoted as L)
- 3) Resistor (small value for practical considerations)
- 4) DC Power Supply
- 5) Oscilloscope

3 THEORY

An LC circuit consists of an inductor (L) and a capacitor (C) connected in parallel. When a charged capacitor is connected to an inductor, energy oscillates between the capacitor's electric field and the inductor's magnetic field. This oscillatory behavior is governed by the second-order differential equation:

$$L \frac{d^2 q}{dt^2} + R \frac{dq}{dt} + \frac{q}{C} = 0,$$

where $q(t)$ is the charge on the capacitor as a function of time.

The natural frequency of oscillation is given by:

$$\omega_n = \frac{1}{\sqrt{LC}},$$

where: - L is the inductance in henries (H), - C is the capacitance in farads (F).

For an ideal LC circuit (no resistance), the damping ratio ($\xi = 0$) indicates purely oscillatory behavior. However, in practical circuits, resistance (R) introduces damping, and the damping ratio becomes:


$$\xi = \frac{R}{2} \sqrt{\frac{C}{L}}.$$

From this, we get,

$$\omega = \omega_n \sqrt{1 - \xi^2}$$

where, ω is the oscillating frequency

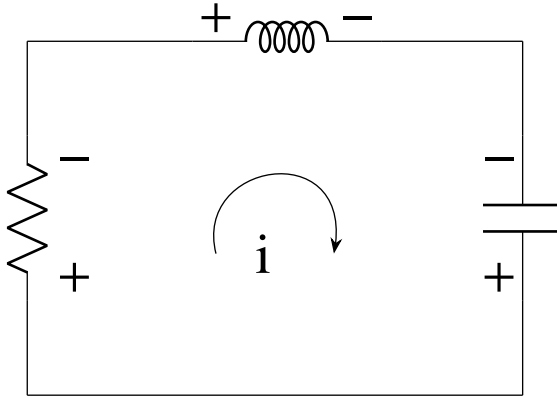For experimental analysis, we monitor voltage waveforms using an oscilloscope. The observed oscillation frequency can be compared with theoretical calculations to validate the model.



4 PROCEDURE

- 1) Precharge the Capacitor:
 - Connect the capacitor to a 5V DC power supply.
 - Once charged, disconnect it carefully without discharging.
- 2) Construct the LC Circuit:
 - Connect the charged capacitor in parallel with the largest available inductor.
 - Ensure minimal resistance in wiring.
- 3) Capture Transient Response:
 - Use an oscilloscope to monitor voltage across the capacitor.
 - Observe natural oscillations.
- 4) Calculate Theoretical Values:
 - Compute natural frequency ($\Omega_n = 1/\sqrt{LC}$).
 - Estimate damping ratio ($\xi = R/2\sqrt{\frac{C}{L}}$) if resistance is non-negligible.
- 5) Compare with Experimental Results:
 - Extract oscillation frequency from oscilloscope data.
 - Compare with theoretical calculations.

5 OBSERVATIONS

We use $1nF$ capacitor with a $2.2mH$ inductor. This gives,

$$\omega_n = \frac{1}{\sqrt{LC}} = 9.94053 \times 10^5 \text{ rad/s}$$

Given, 10% error in L , and 20% error in C ,

Tolerance is given by,

$$\frac{\Delta\omega_n}{\omega_n} = \frac{1}{2} \left(\frac{\Delta L}{L} + \frac{\Delta C}{C} \right)$$

$$\frac{\Delta\omega_n}{\omega_n} = 0.15$$

Giving us a tolerance of 15%

$$\omega_n = (9.94 \pm 1.49) \times 10^5 \text{ rad/s}$$

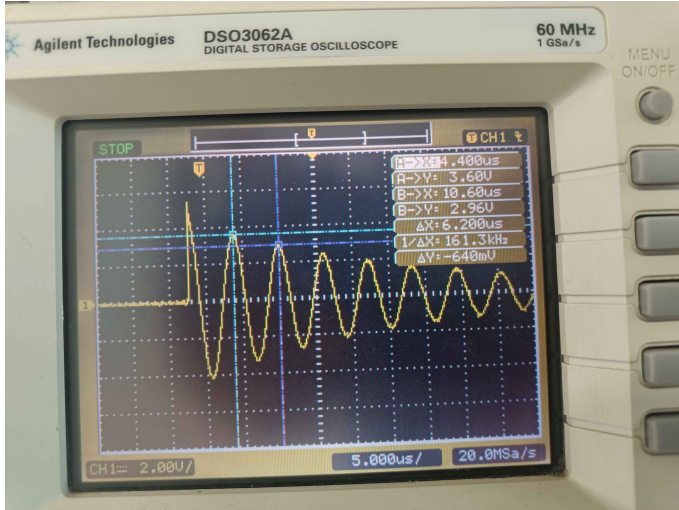


Fig. 1: Transient Response of LC [$L = 2.2\text{mH}$, $C = 560\text{pF}$]

Above reading is across the inductor. Taking reading across the capacitor was impractical as it discharged quick before the oscillation could begin. From the observation,

$$T = 6.2\mu\text{s}$$

$$\omega = \frac{2\pi}{T} = 1.013 \times 10^6 \text{ rad/s}$$

We know that,

$$\omega < \omega_n$$

Thus, we assume ω_n takes values from 1.013×10^6 to $1.143 \times 10^6 \text{ rad/s}$

Damping ratio is given by,

$$\xi = \sqrt{1 - \left(\frac{\omega}{\omega_n}\right)^2}$$

$$\xi_{max} = 0.4631$$

We can observe that damping ratio is less than 1, implying it is underdamped
The internal resistance in the circuit is given by,

$$R_{max} = 2\xi_{max} \sqrt{\frac{L}{C}}$$

$$R_{max} = 2.038k\Omega$$

To find the exact value of R , we can use the peak value. From the observation,

$$V(t = T) = V_0 e^{-\alpha T}$$

$$V_0 e^{-\alpha T} = 680mV$$

$$\alpha = 5.2984 \times 10^4 rad/s$$

$$R = 233\Omega$$

6 PRECAUTIONS

- 1) Make sure not to accidentally discharge the capacitor
- 2) Make sure the DC generator is connected to ground properly
- 3) Use a push button for shorting the inductor and capacitor
- 4) Repeat the experiment multiple times to be sure of the reading as it is a sensitive measurement