

# Experiment 2=3

S A Aravind Eswar and Eshan Sharma

## 1 AIM

Study and plot Bode plot of magnitude and phase response for 1-stage, 2-stage, 3-stage RC Low pass filter.

## 2 MATERIALS AND APPARATUS REQUIRED

- 1) 3 Resistors ( $1k\Omega$  used)
- 2) 3 Capacitors ( $0.1\mu F$  used)
- 3) Bread Board
- 4) Function Generator
- 5) Oscilloscope

## 3 THEORY

The transfer function of a 1-stage RC circuit would be the following,

$$\mathbf{H}(s) = \frac{1}{1 + sRC}$$

where,

$$s = j\omega$$

expanding, we get,

$$\mathbf{H}(s) = \frac{1}{\sqrt{1 + (\omega RC)^2}} e^{j\theta}$$

where,

$$\theta = \tan^{-1}(-\omega RC)$$

Applying logarithm on both sides, we get,

$$\begin{aligned} \log \mathbf{H}(s) &= \log \left( \frac{1}{\sqrt{1 + (\omega RC)^2}} e^{j \tan^{-1}(-\omega RC)} \right) \\ &= -\frac{1}{2} \log(1 + (\omega RC)^2) + j \tan^{-1}(-\omega RC) \end{aligned}$$

Calculating Amplitude gain,

$$A = 20 \log (|\mathbf{H}(s)|)$$

$$A = -10 \log \left( 1 + (\omega RC)^2 \right)$$

This gives the exact equation for Bode plot of the amplitude gain.

For phase difference,

$$\theta = 20 \tan^{-1} (-\omega RC)$$

Similarly,

The transfer function of 2-stage RC circuit would be,

$$\mathbf{H}(s) = \left( \frac{1}{1 - (\omega RC)^2 + 3sRC} \right)$$

And following this, we get,

$$\log \mathbf{H}(s) = -\frac{1}{2} \log \left( (1 - (\omega RC)^2)^2 + (3\omega RC)^2 \right) + j \tan^{-1} \left( \frac{-3\omega RC}{1 - (\omega RC)^2} \right)$$

And,

The transfer function for 3-state RC circuit is given as,

$$\mathbf{H}(s) = \left( \frac{1}{(sRC)^3 + 5(sRC)^2 + 6sRC + 1} \right)$$

And following that we get,

$$\log \mathbf{H}(s) = -\frac{1}{2} \log \left( (1 - 5(\omega RC)^2)^2 + (6\omega RC - (\omega RC)^3) \right) + j \tan^{-1} \left( -\omega RC \frac{6 - (\omega RC)^2}{1 - 5(\omega RC)^2} \right)$$

#### 4 PROCEDURE

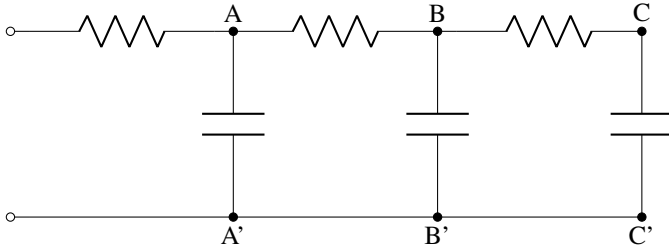


Fig. 1: Circuit Diagram

- 1) Make connections as given in fig. 1

- 2) Give input **V<sub>in</sub>** in the open end.
- 3) Measure Voltage across  $A - A'$  and Phase difference between input voltage and output voltage for 1 cascade circuit analysis.
- 4) Record observations for multiple input frequencies.
- 5) Repeat the experiment for  $B - B'$  and  $C - C'$  for 2 cascade and 3 cascade circuit analysis respectively.
- 6) Compare the theoreical caltuations and observed values.

### 5 OBSERVATIONS

$f$	$V_{out}$	$\Delta t$
10Hz	5.001V	5.6ms
100Hz	5.001V	560 $\mu$ s
500Hz	5.001V	300 $\mu$ s
1000Hz	3.201V	96 $\mu$ s
5000Hz	1.441V	31.2 $\mu$ s
10kHz	880mV	18.4 $\mu$ s
50kHz	200mV	4.48 $\mu$ s
100kHz	104mV	2.2 $\mu$ s
500kHz	30mV	—
1MHz	16mV	—

TABLE I: Obsereved 1 Cascade Circuit Response

$f$	$V_{out}$	$\Delta t$
10Hz	5.001V	5.2ms
50Hz	5.001V	520 $\mu$ s
100Hz	5.001V	320 $\mu$ s
500Hz	4.401V	216 $\mu$ s
1kHz	3.001V	184 $\mu$ s
5kHz	580mV	68 $\mu$ s
10kHz	184mV	40 $\mu$ s
50kHz	16mV	10.8 $\mu$ s

TABLE II: Obsereved 2 Cascade Circuit Response

$f$	$V_{out}$	$\Delta t$
10Hz	4.601V	1.6ms
50Hz	5.001V	200 $\mu$ s
100Hz	5.001V	220 $\mu$ s
1kHz	3.001V	176 $\mu$ s
5kHz	120mV	—
10kHz	30mV	—

TABLE III: Observed 3 Cascade Circuit Response

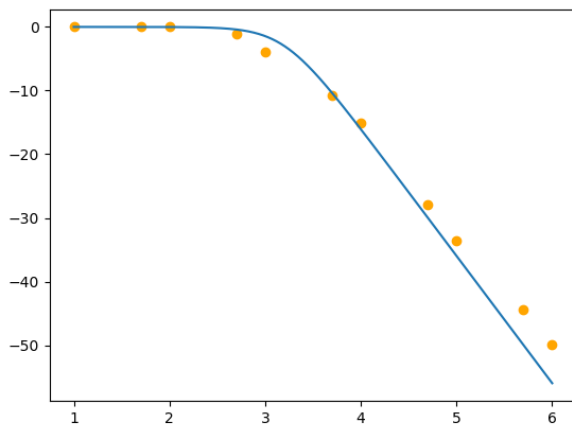


Fig. 2: Amplitude graph for 1 cascade response

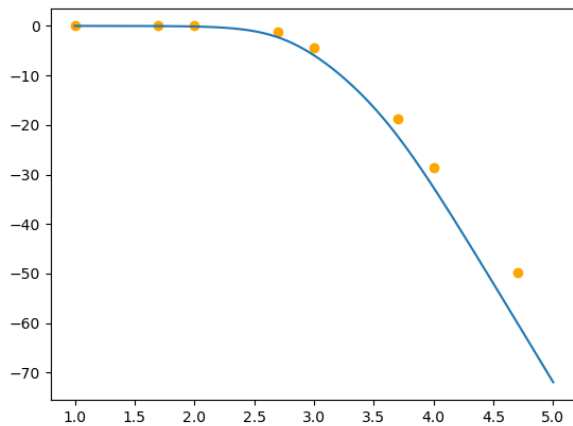


Fig. 3: Amplitude graph for 2 cascase response

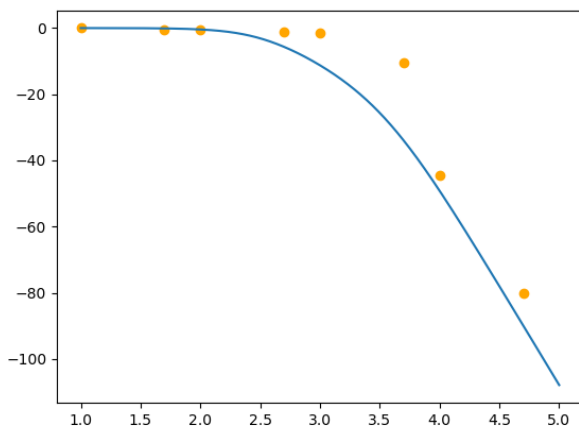


Fig. 4: Amplitude graph for 3 cascase response

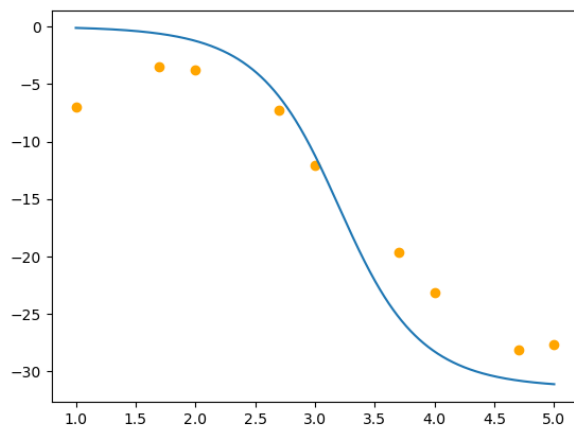


Fig. 5: Phase graph for 1 cascade response

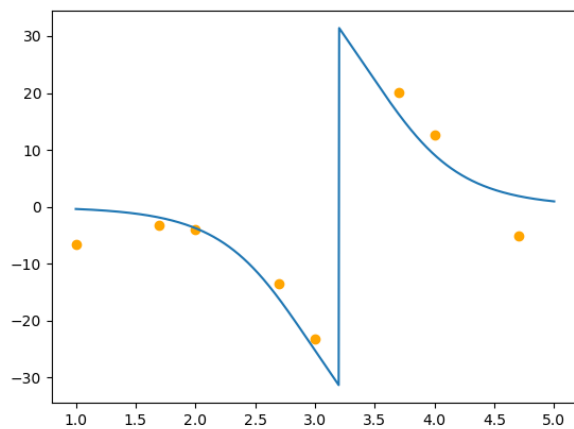


Fig. 6: Phase graph for 2 cascade response

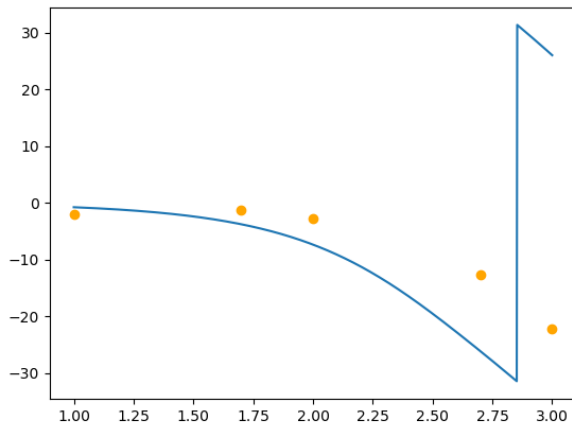


Fig. 7: Phase graph for 2 cascade response